

Discrete IGBT

## Application Manual

## Cautions

This manual contains the product specifications, characteristics, data, materials, and structures as of December 2025.

The contents are subject to change without notice for specification changes or other reasons. When using a product listed in this manual, be sure to obtain the latest specifications.

Fuji Electric Co., Ltd. is constantly making every endeavor to improve the product quality and reliability. However, on rare occasions, semiconductor products may fail or malfunction. To prevent accidents causing injury or death, damage to property like by fire, and other social damage resulted from a failure or malfunction of the Fuji Electric Co., Ltd. semiconductor products, take measures to ensure safety such as redundant design, fire spread prevention design, and malfunction prevention design.

The contents described in this specification never ensure to enforce the industrial property and other rights, nor license the enforcement rights.

The products described in this specification are not designed nor made for being applied to the equipment or systems used under life-threatening situations. When you consider applying the product of this specification to particular use, such as vehicle-mounted units, shipboard equipment, aerospace equipment, medical devices, atomic control systems and submarine relaying equipment or systems, Fuji Electric is not responsible for the applicability.

The data and other information contained in this specification are guaranteed for the product, but do not guarantee the characteristics and quality of the equipment applying this product. When using this product, please evaluate it in the application in which it will be used, and then judge its applicability at user's own risk. Fuji Electric is not responsible for the applicability.

## Chapter 5 Protection Circuit Design

1. Short Circuit (Overcurrent) Protection	5-2
2. Overvoltage Protection	5-8

This chapter describes about the protection circuit design.

## 1. Short Circuit (Overcurrent) Protection

### 1.1 Short circuit withstand capability

If the equipment experiences a short circuit due to an abnormal condition, the IGBT's collector current  $I_C$  rises, and once it exceeds a certain threshold, the C-E voltage  $V_{CE}$  abruptly increases. This characteristic limits  $I_C$  during a short circuit to below a certain level, but subjects the IGBT to high voltage and large current. If this state persists, the IGBT will be destroyed. The duration that an IGBT can survive such a condition without damage is specified as short circuit withstand capability.

The discrete IGBT XS series is optimized for low switching loss and low saturation voltage, traits that trade off against short circuit withstand capability. Consequently, short circuit withstand capability is not guaranteed for this series. Do not use XS series devices in circuits where short circuit is anticipated.

The concept of short-circuit withstand capability for arm short circuit and output short circuit is explained below.

#### 1.1.1 Arm short circuit

Fig. 5-1 shows an arm short circuit test circuit and waveform example. As for the arm short circuit, the  $I_C$  rises sharply at the start of the short circuit and drops slightly after saturation. The short circuit (saturation) current value  $I_{SC}$  is determined by  $V_{GE}$ , device output characteristics, and  $T_{vj}$ , and is almost independent of  $V_{DC}$ ,  $R_G$ , and PW.

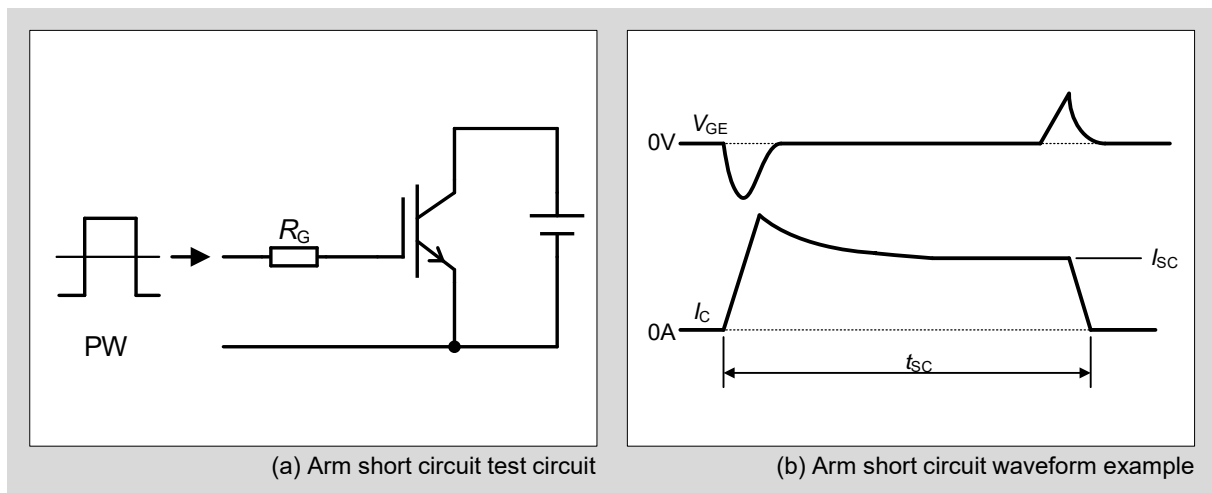


Fig. 5-1 Arm short circuit test circuit and waveform

### 1.1.2 Output short circuit

Fig. 5-2 shows the output short circuit test circuit and waveform example. In the output short circuit, the short circuit wire has inductance component, thus the current waveform at the start of the short circuit is different from that in the case of the arm short circuit. In this case, the current rise rate  $d_i/d_t$  can be expressed as follows.

$$d_i/d_t = V_{DC}/L \text{ (A/sec)}$$

If the time from the start of the short circuit is given as  $t$  (sec),  $I_C$  can be expressed as follows.

$$I_C = d_i/d_t \cdot t \text{ (A)}$$

The  $I_C$  peak value depends on the inductance and the drive circuit (transient  $V_{GE}$  rise). After reaching the peak value and saturating,  $V_{CE}$  rises sharply. From here, it becomes the same situation with an arm short circuit.

The short circuit withstand capability in the case of output short circuit is shown in Fig. 5-2(b) as (PW). During  $I_C$  rise,  $V_{DC}$  is applied to the inductance  $L$ , and the voltage across the IGBT is about  $V_{CE(sat)}$ , thus the load on the IGBT is extremely low compared to the arm short circuit. Therefore, this period is not included in the short circuit withstand capability.

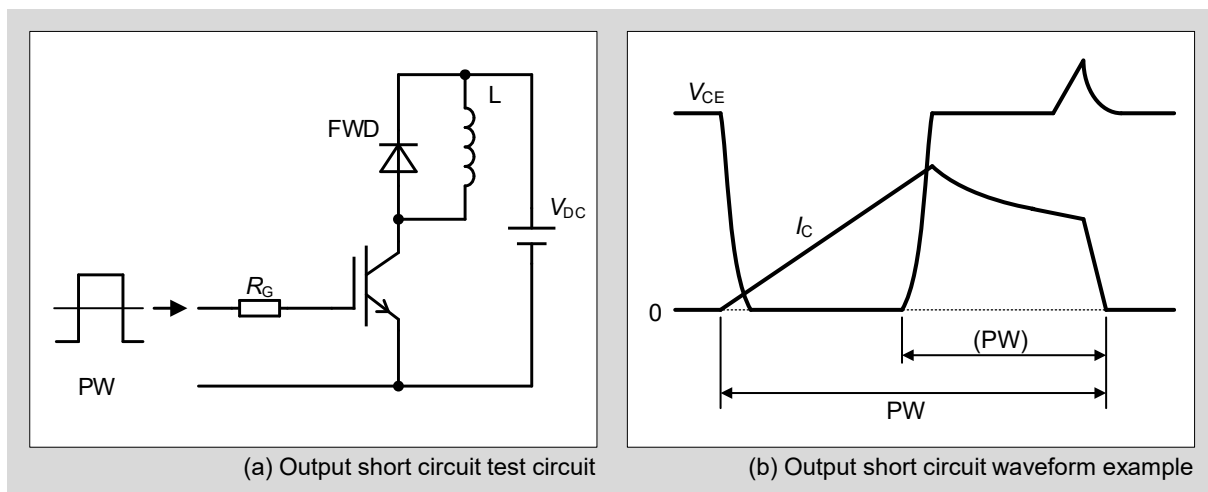
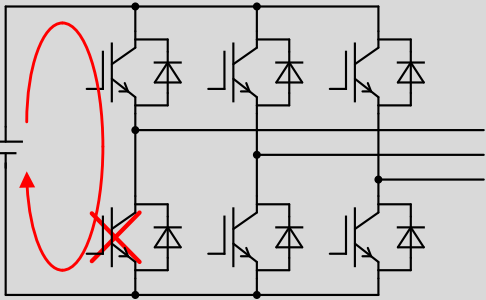
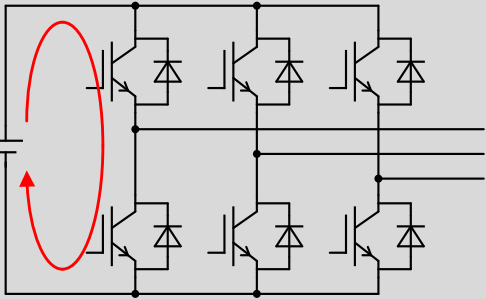
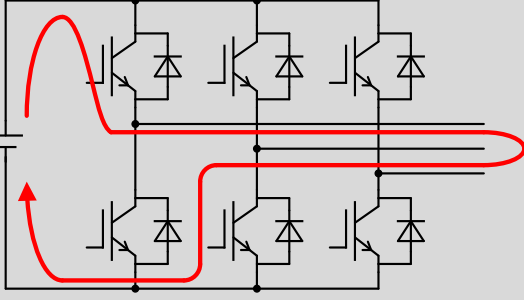
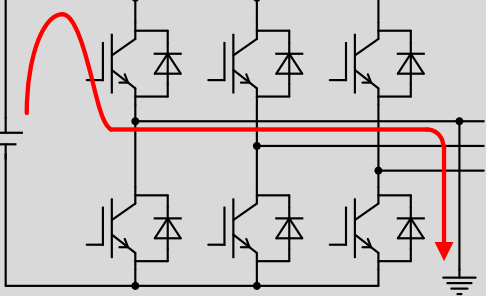


Fig. 5-2 Output short circuit test circuit and waveform

## 1.2 Short circuit modes and causes

Table 5-1 shows the short circuit modes and causes that occur in inverters.

Table 5-1 Short circuit modes and causes

Short circuit mode	Cause
<p>Arm short circuit</p> 	IGBT or diode destruction.
<p>Series arm short circuit</p> 	Control circuit / drive circuit failure or malfunction due to noise.
<p>Output short circuit</p> 	Miswiring or dielectric breakdown of load
<p>Ground fault</p> 	Miswiring or dielectric breakdown of load

### 1.3 Short-Circuit Detection Methods

The following describes methods for detecting a short circuit. Note that these techniques are only valid for the V-series IGBTs. Do not use the XS-series in circuits where a short circuit may occur.

#### 1.3.1 Detection by overcurrent detector

As mentioned, in the event of a short circuit, the IGBT must be turned off as soon as possible. Therefore, the time from short circuit detection to the completion of turn-off must be as short as possible.

Since the IGBT turns off very fast, if the short circuit is turned off with a normal gate drive signal, a large surge voltage will be generated, and the IGBT may be destroyed by overvoltage (RBSOA destruction). Therefore, it is recommended to turn off the IGBT slowly (soft turn-off).

Fig. 5-3 shows the overcurrent detectors position in an inverter circuit, and Table 5-2 shows the features and the types of short circuit that can be detected by each method. Consider what kind of protection is necessary and select the most appropriate form of detection.

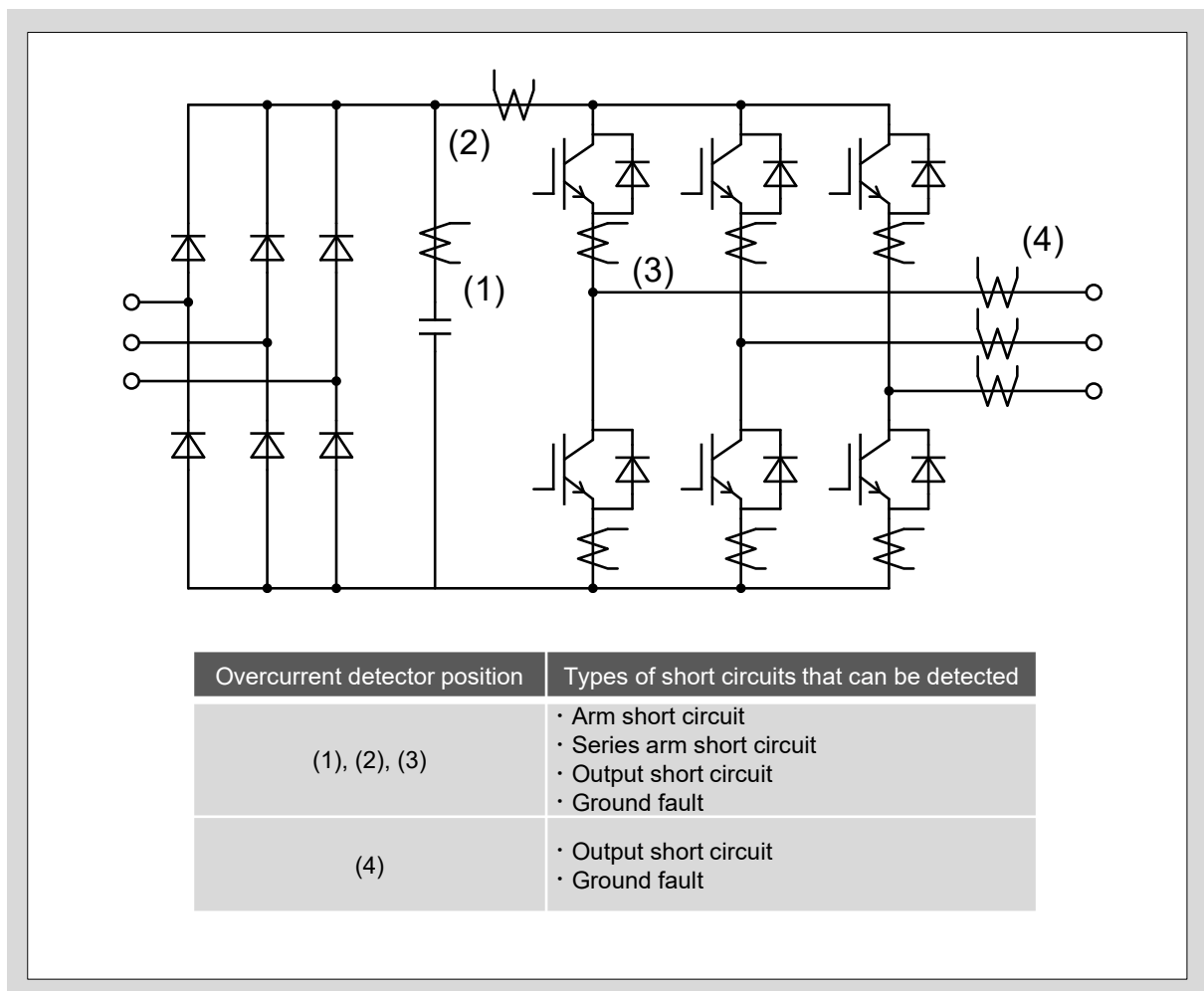


Fig. 5-3 Overcurrent detector position

Table 5-2 Overcurrent detector positions and their features

Overcurrent detector position	Feature	Types of short circuits that can be detected
In series with smoothing capacitor Fig. 5-3/(1)	<ul style="list-style-type: none"> <li>• AC current transducer can be used</li> <li>• Low detection precision</li> </ul>	<ul style="list-style-type: none"> <li>• Arm short circuit</li> <li>• Series arm short circuit</li> <li>• Output short circuit</li> <li>• Ground fault</li> </ul>
At inverter input Fig. 5-3/(2)	<ul style="list-style-type: none"> <li>• DC current transducer is required</li> <li>• Low detection precision</li> </ul>	<ul style="list-style-type: none"> <li>• Arm short circuit</li> <li>• Series arm short circuit</li> <li>• Output short circuit</li> <li>• Ground fault</li> </ul>
In series with each IGBT Fig. 5-3/(3)	<ul style="list-style-type: none"> <li>• DC current transducer is required</li> <li>• High detection precision</li> </ul>	<ul style="list-style-type: none"> <li>• Arm short circuit</li> <li>• Series arm short circuit</li> <li>• Output short circuit</li> <li>• Ground fault</li> </ul>
At inverter output Fig. 5-3/(4)	<ul style="list-style-type: none"> <li>• AC current transducer can be used for equipment with high frequency output</li> <li>• High detection precision</li> </ul>	<ul style="list-style-type: none"> <li>• Output short circuit</li> <li>• Ground fault</li> </ul>

### 1.3.2 Detection by $V_{CE(sat)}$

This method can protect against all types of short circuit shown in Table 5-1. Since the operations from overcurrent detection to protection are done on the drive circuit side, this method offers the fastest protection possible. Fig. 5-4 shows an example of short circuit protection circuit using  $V_{CE(sat)}$  detection method.

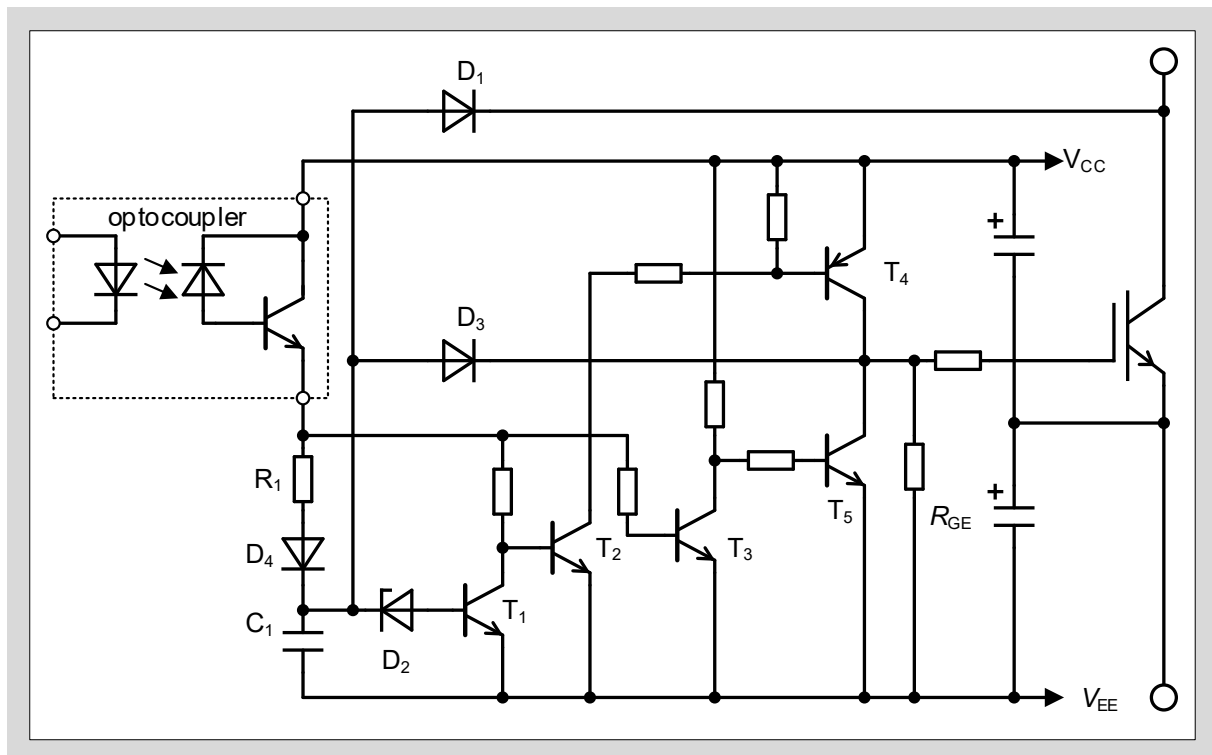


Fig. 5-4 Short-circuit protection circuit using  $V_{CE(sat)}$  detection method

This circuit uses diode  $D_1$  to constantly monitor the C-E voltage.

When the optocoupler is turned on, transistors  $T_2$  and  $T_4$  are turned on and a positive gate voltage is applied to the IGBT. Also, the capacitor  $C_1$  is charged through the resistor  $R_1$  and diode  $D_4$ . The operation changes depending on the voltage of capacitor  $C_1$ .

**【Short circuit protection operation】**

If a short circuit occurs after the IGBT is turned on, the  $V_{CE}$  of the IGBT rises. When  $V_{CE}$  becomes higher than the voltage of  $[C_1 - D_1 (V_F - V_{EE})]$ , diode  $D_1$  is turned off and the voltage of capacitor  $C_1$  rises again. When the voltage of capacitor  $C_1$  becomes higher than  $[V_Z$  of Zener diode  $D_2 + V_{BE}$  of transistor  $T_1]$ , short circuit protection operates.

In the short circuit protection operation, a current flows through Zener diode  $D_2$  to the base of transistor  $T_1$ , turning it on. When transistor  $T_1$  is turned on, transistors  $T_2$  and  $T_4$  are turned off, and the applied positive gate voltage is cut off. Since the optocoupler is on, the transistor  $T_3$  is on and transistor  $T_5$  is off. Since the transistors  $T_4$  and  $T_5$  are turned off at the same time, the gate accumulated charge is slowly discharged through the  $R_{GE}$ . This effect can suppress the generation of excessive surge voltage when the IGBT turns off. Fig. 5-5 shows an example of the short circuit protection waveform.

**【Normal operation】**

After the IGBT is turned on, the IGBT is kept on by keeping the voltage of capacitor  $C_1$  below  $[V_Z$  of the Zener diode  $D_2 + V_{BE}$  of transistor  $T_1]$ . When the optocoupler is turned off, the transistors  $T_2$ ,  $T_4$  turn off, transistor  $T_3$  turns off, and transistor  $T_5$  turns on, applying a negative gate voltage to the IGBT. The charge on capacitor  $C_1$  is discharged through diode  $D_3$  and transistor  $T_5$  and reset to 0V. As can be seen from the above operation sequence, short circuit protection is monitored on each pulse.

## 2. Overvoltage Protection

### 2.1 Cause of overvoltage and suppression methods

#### 2.1.1 Cause of overvoltage

Due to the high switching speed of IGBTs, during turn-off or FWD reverse recovery, the current change rate  $di/dt$  is very high. Therefore, the circuit wiring inductance around the module  $L_S$  can generate a high surge voltage  $V_{CEP} = L_S \cdot (di/dt)$ .

Fig. 5-5 shows a chopper circuit for measuring the turn-off surge voltage, and Fig. 5-6 shows the switching waveforms.

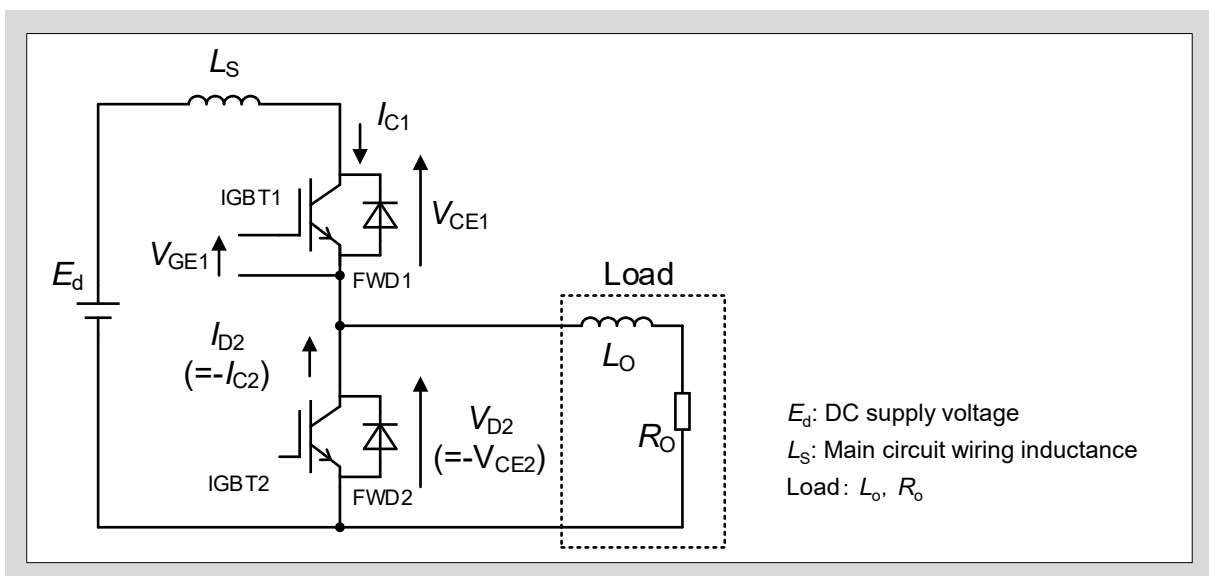


Fig. 5-6 Chopper circuit

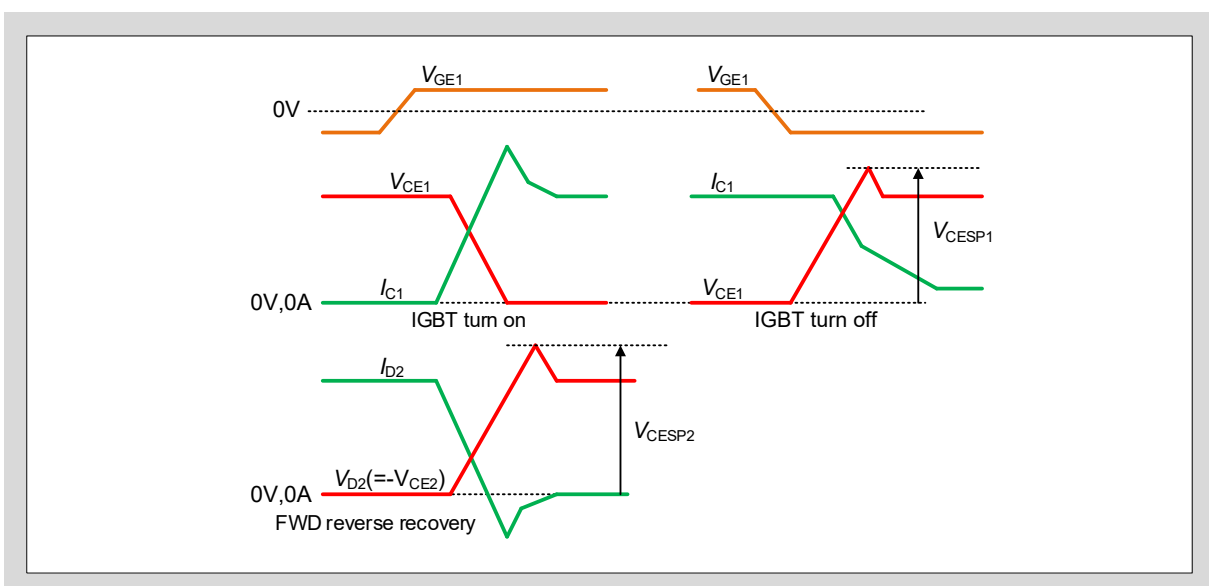


Fig. 5-7 Switching waveforms

Surge voltage is generated when the IGBT turns off: the rapid change in main-circuit current induces a high voltage across the stray inductance  $L_s$  of the main circuit.

The peak value of turn-off surge voltage  $V_{CESP}$  can be calculated as follows.

$$V_{CESP} = V_{CC} + (-L_s \cdot \frac{di_c}{dt}) \quad di_c/dt: \text{Maximum } I_C \text{ change rate at turn-off}$$

If  $V_{CESP}$  exceeds the  $V_{CES}$  rating, the IGBT will be destroyed.

### 2.1.2 Overvoltage suppression methods

The following methods are available for suppressing turn-off surge voltage.

- Suppress the surge voltage by adding a protection circuit such as a snubber circuit to the IGBT. Use a film capacitor and place it as close as possible to the IGBT in order to suppress high frequency surge voltage.
- Adjust the  $-V_{GE}$  and  $R_G$  of the drive circuit in order to reduce the  $di/dt$ . (For details, refer to Chapter 7, 'Gate Drive Circuit Design')
- Place the DC capacitor as close as possible to the IGBT in order to reduce  $L_s$ . Use a low impedance type capacitor.
- Reduce the  $L_s$  of the main circuit and snubber circuit by using thicker and shorter wires. It is also very effective to use laminated bus bars.
- Use an active clamp circuit. The surge voltage is suppressed to approximately equal to the Zener voltage of the Zener diode.

## 2.2 Types of snubber circuits and their features

Snubber circuits can be classified into two types: individual snubber circuit and lump snubber circuit. Individual snubber circuits are connected to each IGBT, while lump snubber circuits are connected between the DC power supply bus and the ground for centralized protection.

### 2.2.1 Individual snubber circuits

Examples of typical individual snubber circuits are as follows.

- RC snubber circuit
- Charge-discharge RCD snubber circuit
- Discharge-suppressing RCD snubber circuit

Table 5-3 shows the schematic and features of each type of individual snubber circuit.

### 2.2.2 Lump snubber circuits

Examples of typical lump snubber circuits are as follows.

- C snubber circuit
- RCD snubber circuit

Lump snubber circuits are becoming increasingly popular due to circuit simplification.

Table 5-4 shows the schematic and features of each type of lump snubber circuit.

Table 5-3 Individual snubber circuits

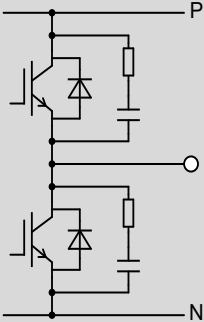
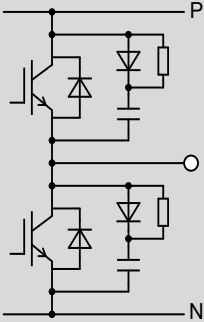
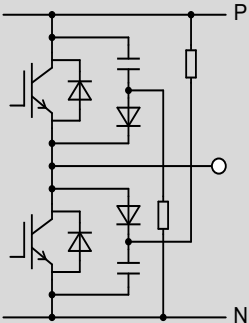
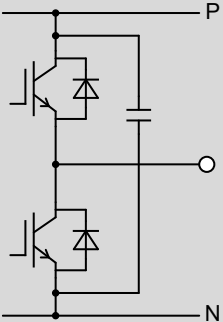
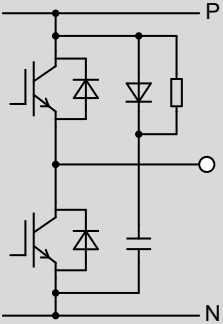
Snubber circuit schematic	Features (Notes)
<p>RC snubber circuit</p> 	<ul style="list-style-type: none"> <li>• The surge voltage suppression effect is greater than that of a lump snubber circuit.</li> <li>• When applied to large capacity IGBTs, the snubber resistance must be low. As a result, the current at turn-on increases and increase the IGBT load.</li> </ul>
<p>Charge-discharge RCD snubber circuit</p> 	<ul style="list-style-type: none"> <li>• Unlike the RC snubber circuit, a snubber diode is added. Thus, snubber resistance can be increased, and decrease the IGBT load at turn-on .</li> <li>• The power dissipation loss by the snubber resistance of this circuit can be calculated as follows.</li> </ul> $P = \frac{L_S \cdot I_o^2 \cdot f}{2} + \frac{C_S \cdot E_d^2 \cdot f}{2}$ <p> <i>L<sub>S</sub></i>: Wiring inductance of main circuit  <i>I<sub>o</sub></i>: Collector current at IGBT turn-off  <i>C<sub>S</sub></i>: Capacitance of snubber capacitor  <i>E<sub>d</sub></i>: DC power supply voltage  <i>f</i>: Switching frequency         </p>
<p>Discharge-suppressing RCD snubber circuit</p> 	<ul style="list-style-type: none"> <li>• Power dissipation loss of snubber circuit is small.</li> <li>• The power dissipation loss by the snubber resistance of this circuit can be calculated as follows.</li> </ul> $P = \frac{L_S \cdot I_o^2 \cdot f}{2}$ <p> <i>L<sub>S</sub></i>: Wiring inductance of main circuit  <i>I<sub>o</sub></i>: Collector current at IGBT turn-off  <i>f</i>: Switching frequency         </p>

Table 5-4 Lump snubber circuits

Snubber circuit schematic	Features (Notes)
<p>C snubber circuit</p> 	<ul style="list-style-type: none"> <li>• This is the simplest snubber circuit.</li> <li>• The LC resonance circuit, which consists of main circuit inductance and snubber capacitor, may cause the C-E voltage to oscillate.</li> </ul>
<p>RCD snubber circuit</p> 	<ul style="list-style-type: none"> <li>• If the snubber diode is selected incorrectly, a high surge voltage will be generated or the voltage may oscillate during reverse recovery of the snubber diode.</li> </ul>

### 2.3 Discharge-suppressing RCD snubber circuit design

The discharge-suppressing RCD snubber circuit is considered the most suitable snubber circuit for IGBT. The basic design method of this circuit is as follows.

#### 2.3.1 Study of applicability

Fig. 5-7 shows the turn-off locus of IGBT with discharge-suppressing RCD snubber circuit.

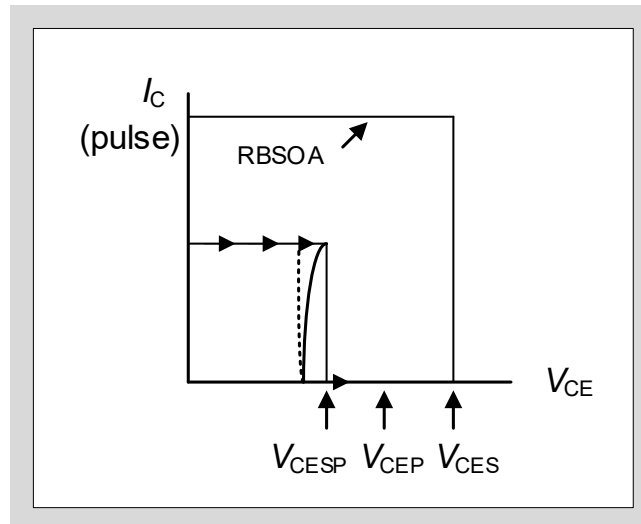


Fig. 5-7 Turn-off locus of IGBT

Fig. 5-8 shows the IGBT turn-off waveform. The discharge-suppressing RCD snubber circuit operates after  $V_{CE}$  of the IGBT exceeds the DC power supply voltage. The ideal operation trajectory is shown by the dotted line.

However, in actual equipment, there is surge voltage at turn-off due to the wiring inductance of the snubber circuit and the transient forward voltage of the snubber diode, thus the actual waveform is as shown by the solid line.

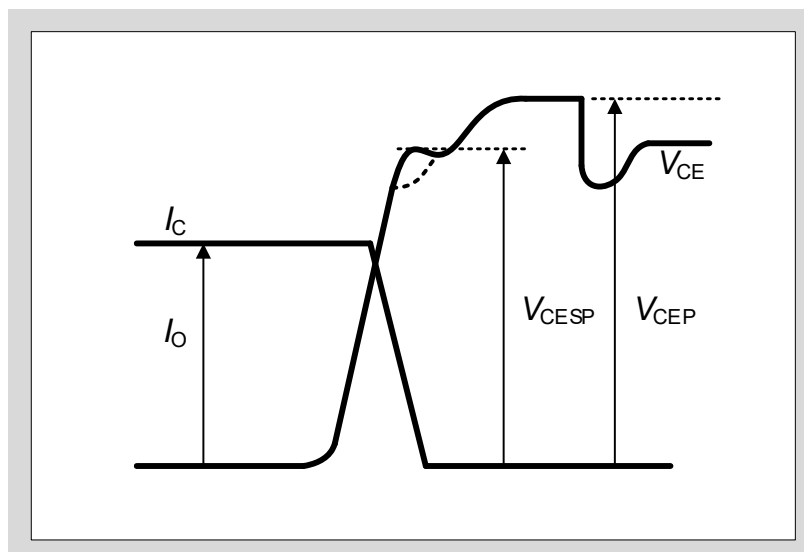


Fig. 5-8 IGBT turn-off waveform

The discharge-suppressing RCD snubber circuits applicability is decided by whether the turn-off locus after applying the snubber circuit is within the RBSOA.

The surge voltage at IGBT turn-off is calculated as follows.

$$V_{CESP} = E_d + V_{FM} + (-L_S \cdot \frac{dI_c}{dt})$$

- $E_d$  :DC power supply voltage
- $V_{FM}$  :Transient forward voltage of snubber diode  
The reference values are as follows.  
600V class: 20 to 30V  
1200V class: 40 to 60V
- $L$  :Snubber circuit wiring inductance
- $dI_c/dt$  :Maximum  $I_c$  change rate at IGBT turn-off

### 2.3.2 Calculating the snubber capacitance ( $C_S$ )

The capacitance of the snubber capacitor is calculated as follows.

$$C_S = \frac{L_S \cdot I_o^2}{(V_{CEP} - E_d)^2}$$

- $L_S$  :Main circuit wiring inductance
- $I_o$  :Collector current at IGBT turn-off
- $V_{CEP}$  :Snubber capacitor peak voltage
- $E_d$  :DC power supply voltage

$V_{CEP}$  must be limited to less than  $V_{CES}$  of the IGBT. Use a snubber capacitor with good high-frequency characteristics such as a film capacitor.

### 2.3.3 Calculating the snubber resistance ( $R_S$ )

The function of the snubber resistor is to discharge the accumulated charge in the snubber capacitor before the next IGBT turn-off. To discharge 90% of the accumulated charge by the next IGBT turn-off, the snubber resistance is calculated as follows.

$$R_S \leq \frac{1}{2.3 \cdot C_S \cdot f}$$

- $R_S$  :Snubber resistance
- $C_S$  :Snubber capacitance
- $f$  :Switching frequency

If the snubber resistance is set too low, the snubber circuit current will oscillate and the peak collector current at the IGBT turn-off will increase. Therefore, set the snubber resistance as high as possible within the calculated range.

Irrespective of the resistance value, the power dissipation of the snubber resistor  $P(R_S)$  is calculated as follows.

$$P(R_S) = \frac{L_S \cdot I_o^2 \cdot f}{2}$$

- $P(R_S)$  :Power dissipation of snubber resistor
- $L_S$  :Main circuit wiring inductance
- $I_o$  :Collector current at IGBT turn-off
- $f$  :Switching frequency

#### **2.3.4 Snubber diode selection**

The transient forward voltage of the snubber diode is one of the cause of surge voltage at IGBT turn-off. If the reverse recovery time of the snubber diode is too long, the power dissipation loss of the snubber diode will also be much higher during high frequency switching. Also, if the reverse recovery of the snubber diode is too hard, then the IGBT C-E voltage will oscillate greatly.

Therefore, select a snubber diode that has a low transient forward voltage, a short reverse recovery time, and a soft reverse recovery.

#### **2.3.5 Snubber circuit wiring precautions**

The snubber circuit wiring inductance is one of the main cause of surge voltage, therefore it is important to reduce the wiring inductance, as well as considering the layout of circuit components.

## 2.4 Overvoltage suppression circuit -example of clamp circuit configuration-

In general, surge voltage can be suppressed by means of decreasing the stray inductance or installing a snubber circuit. However, it may be difficult to suppress the surge voltage under depending on the operating conditions of the equipment. For such cases, it is effective to use active clamp circuits.

Fig. 5-9 shows an example of active clamp circuit. The circuit configuration adds a Zener diode at C-G of the IGBT, and connect a diode in anti-series with the Zener diode.

When voltage exceeding the Zener voltage of the Zener diode is applied on C-E, the Zener diode breakdown and current flows from collector to the IGBT gate. Positive voltage is added to  $V_{GE}$  by this current flowing through  $R_G$ . When  $V_{GE}$  exceeds the gate threshold voltage  $V_{GE(th)}$ ,  $I_C$  flows through the IGBT, and  $V_{CE}$  is clamped to approximately equal to the Zener voltage of the Zener diode. In this way, surge voltage can be suppressed.

On the other hand, since the active clamp circuit turn on the IGBT, the  $di/dt$  at turn-off becomes slower than before the addition of the clamp circuit, resulting in a longer turn-off time (refer to Fig. 5-10). As this will increase the switching loss, make sure to apply the clamp circuit after verifying if this has no problem with the design of the equipment.

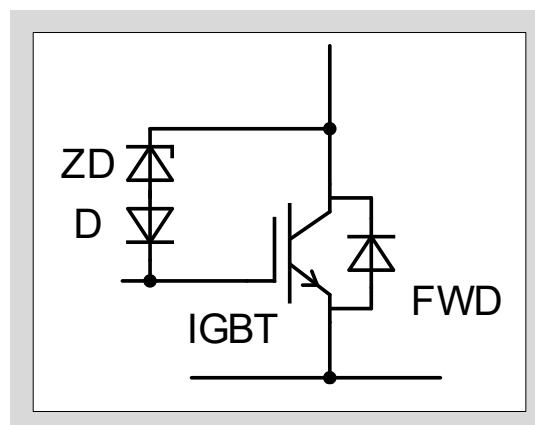


Fig. 5-9 Active clamp circuit

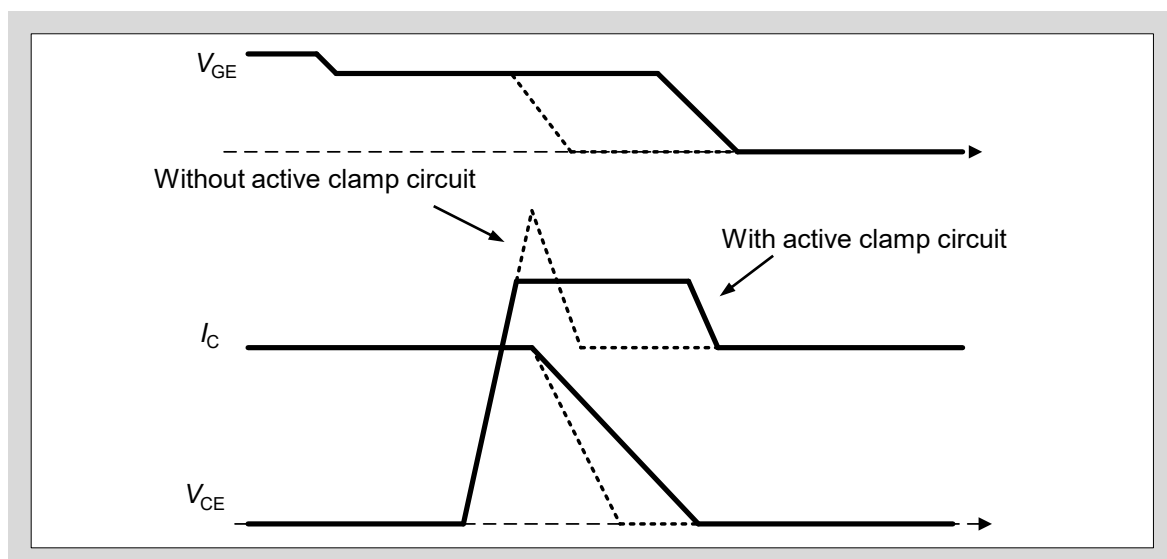


Fig. 5-10 Waveform example when active clamp circuit is applied